

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ


PLC Course

مقرر الحاكمت المنطقية المبرمجة


Lec 5


EX1:

- For the following diagram:

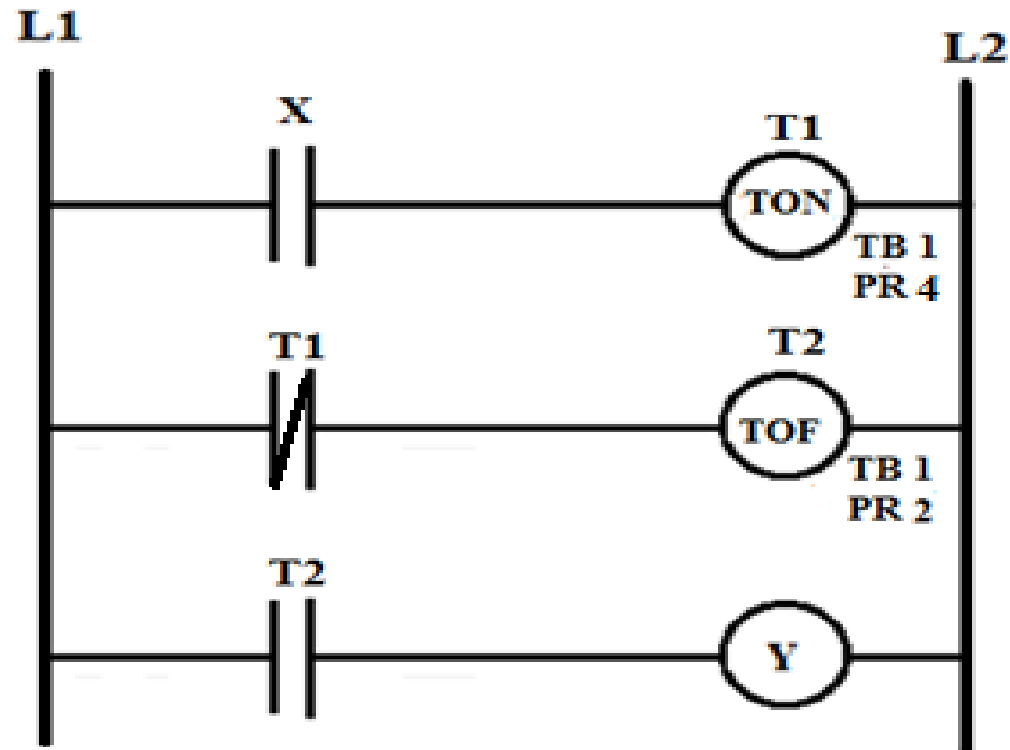


- Using timing diagram, illustrate the states of T1, T2 and Y for the following state of the input switch X:

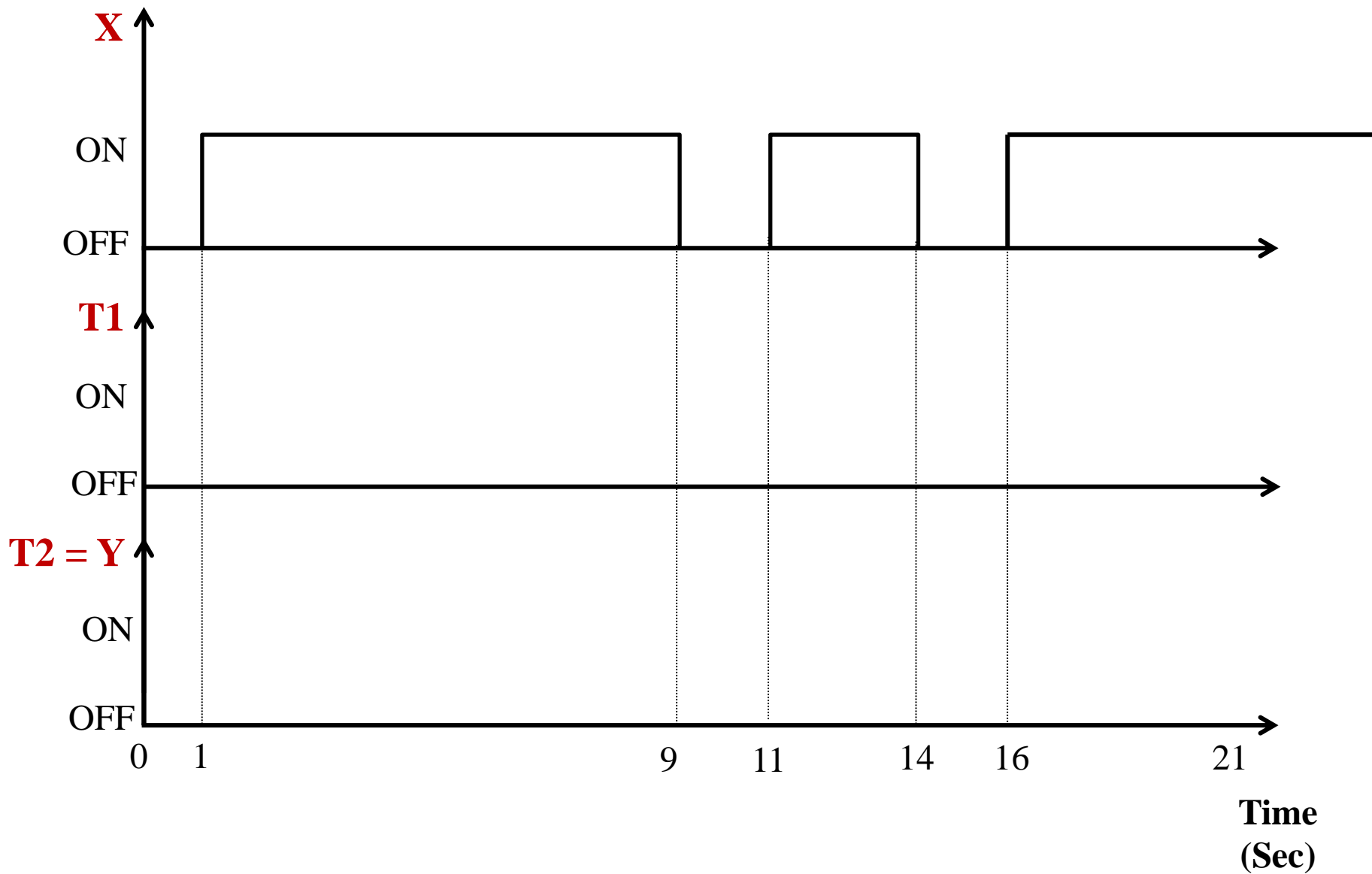

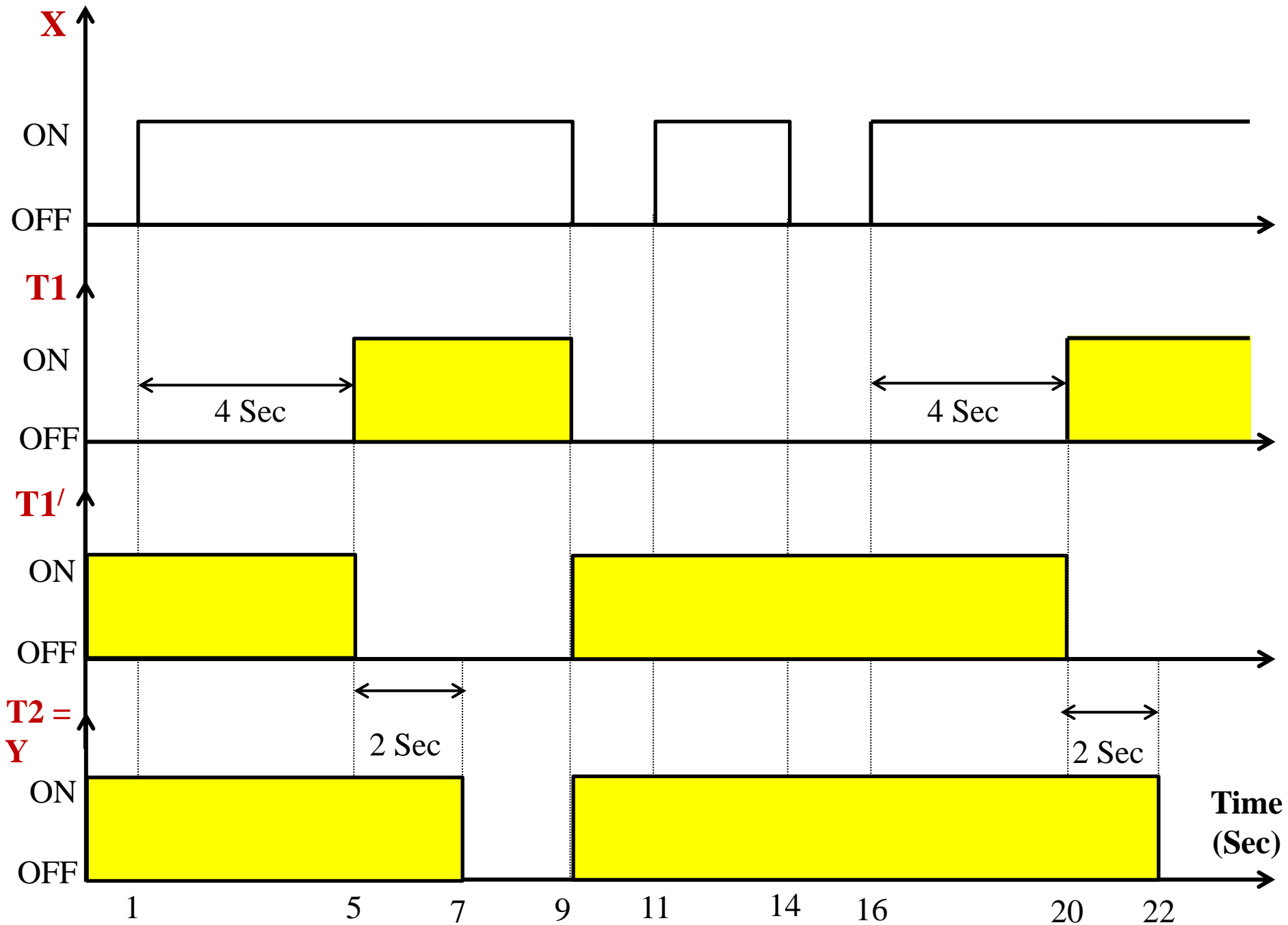


EX2:


- For the following diagram:

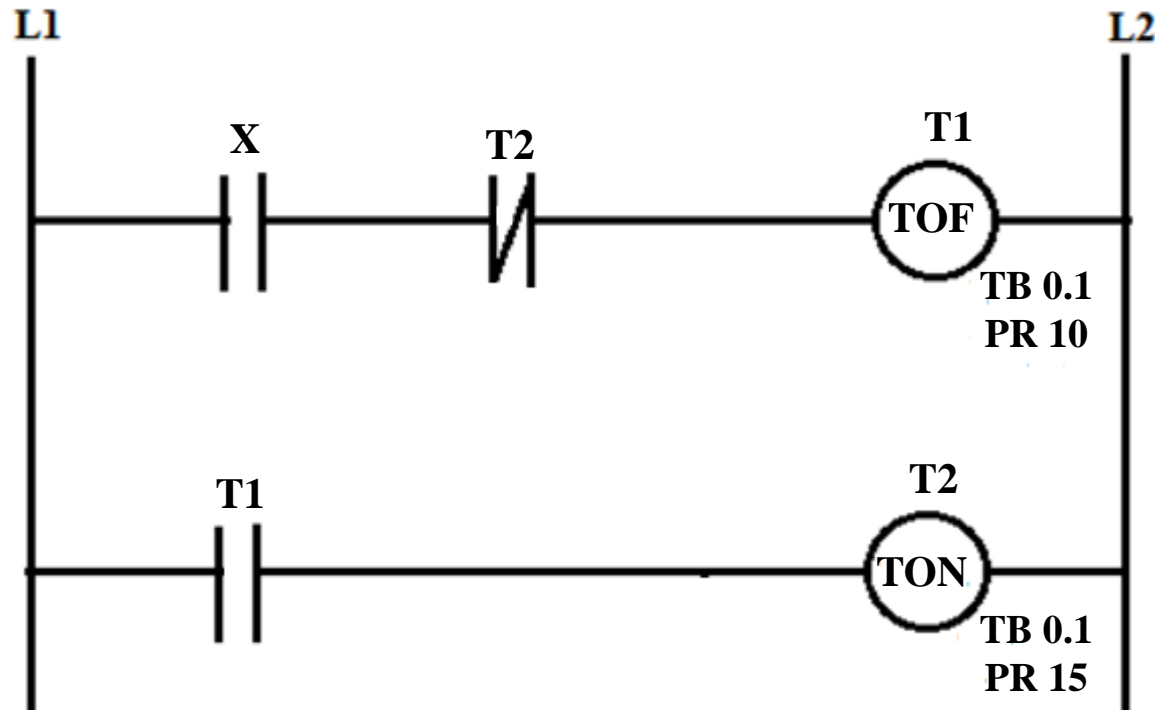

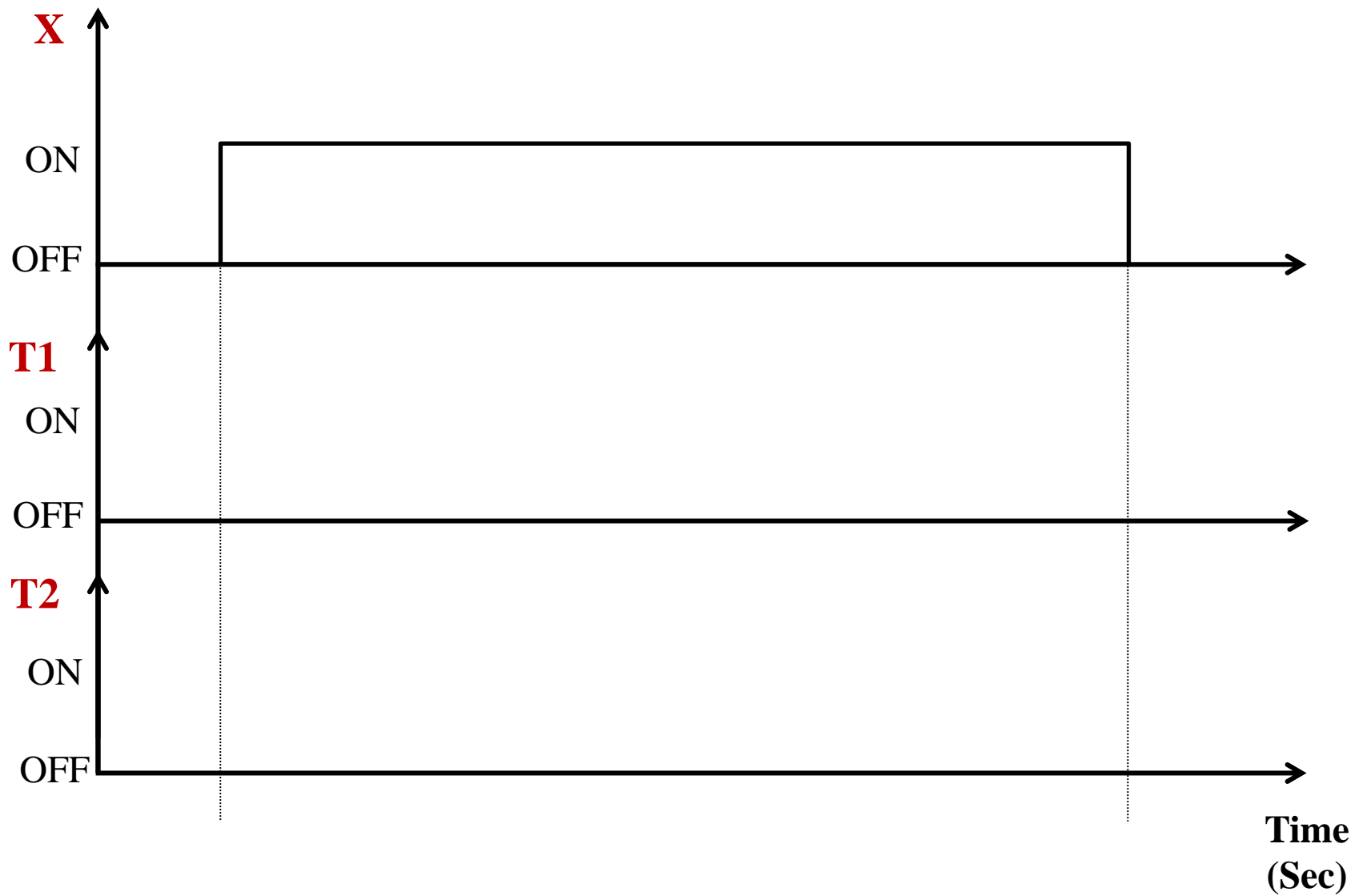- Using timing diagram, illustrate the states of T1 and T2 for the following state of the input switch X:




Timing Diagram

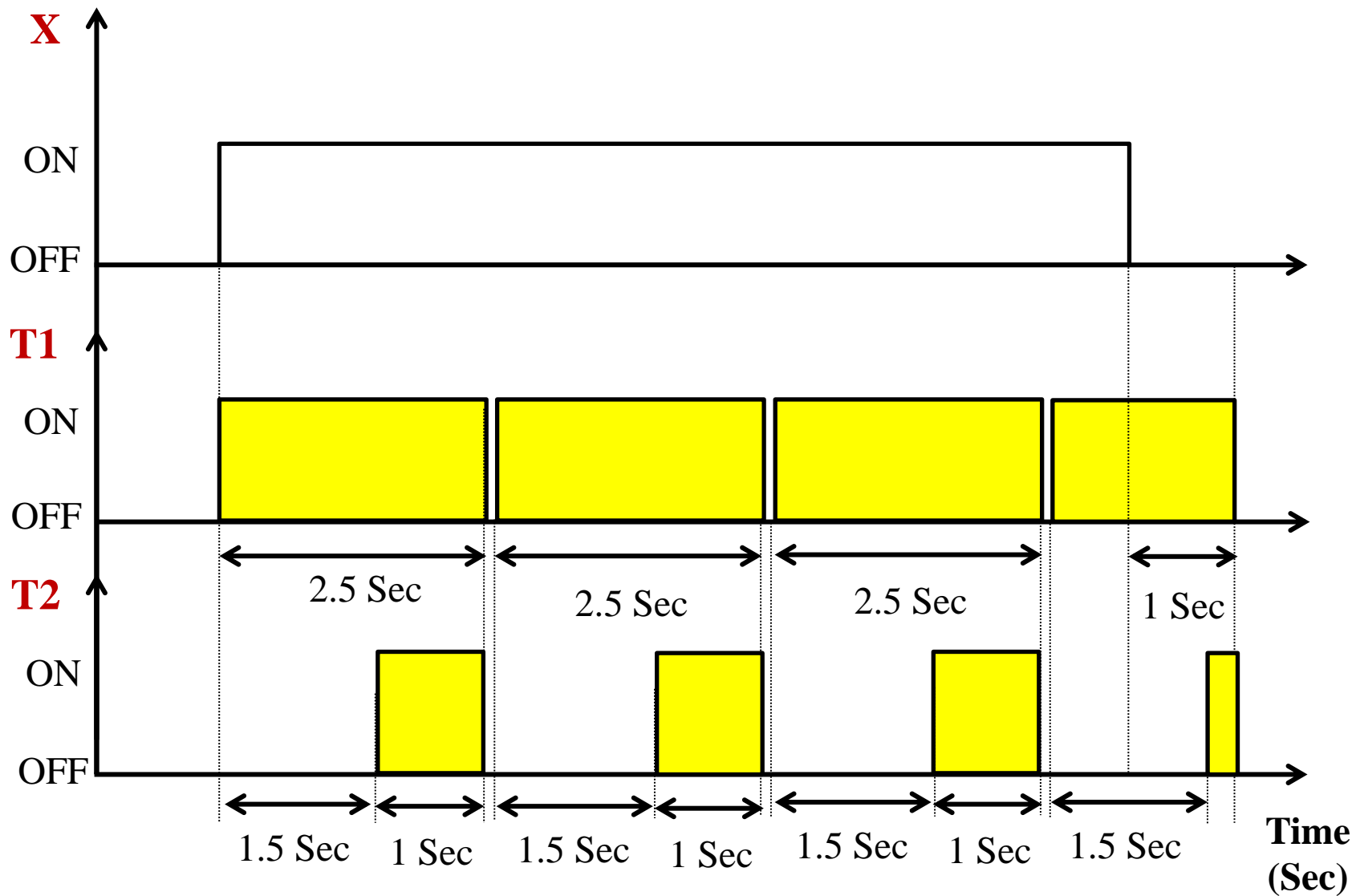


Timing Diagram


EX3:

- For the following diagram:

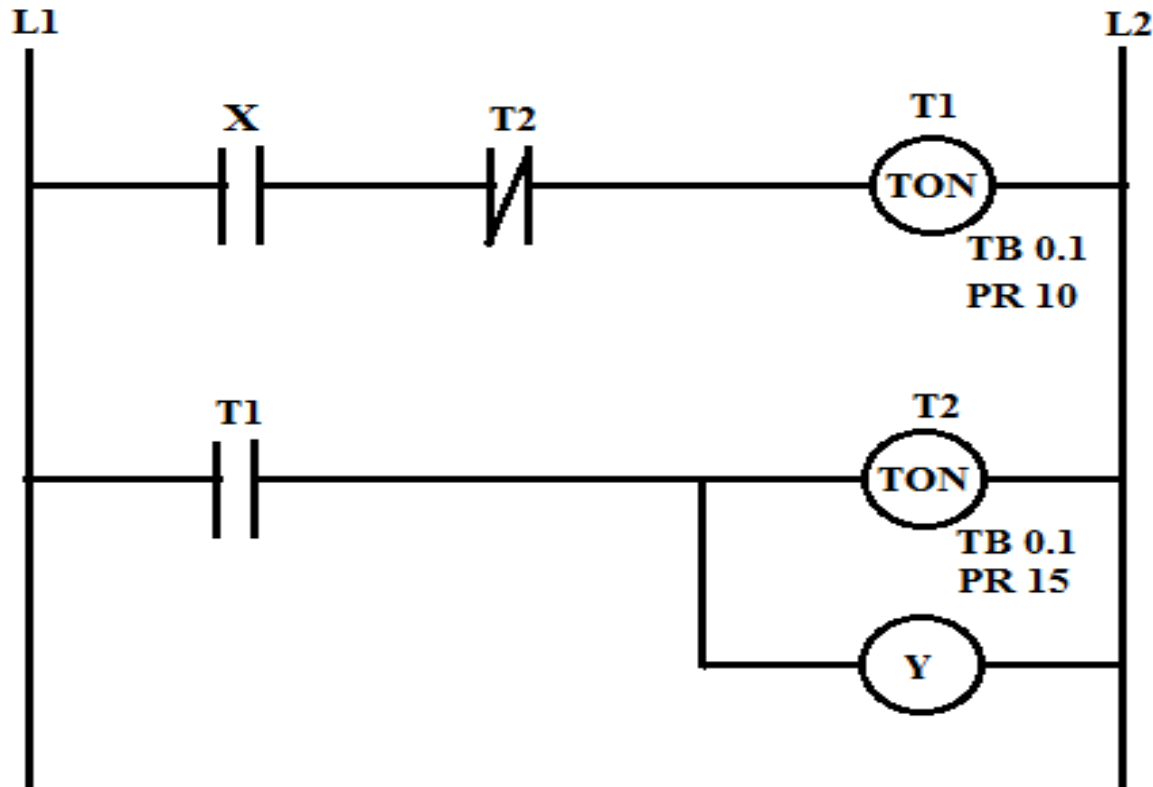


- Using timing diagram, illustrate the states of T1, T2 and Y for the following state of the input switch X:

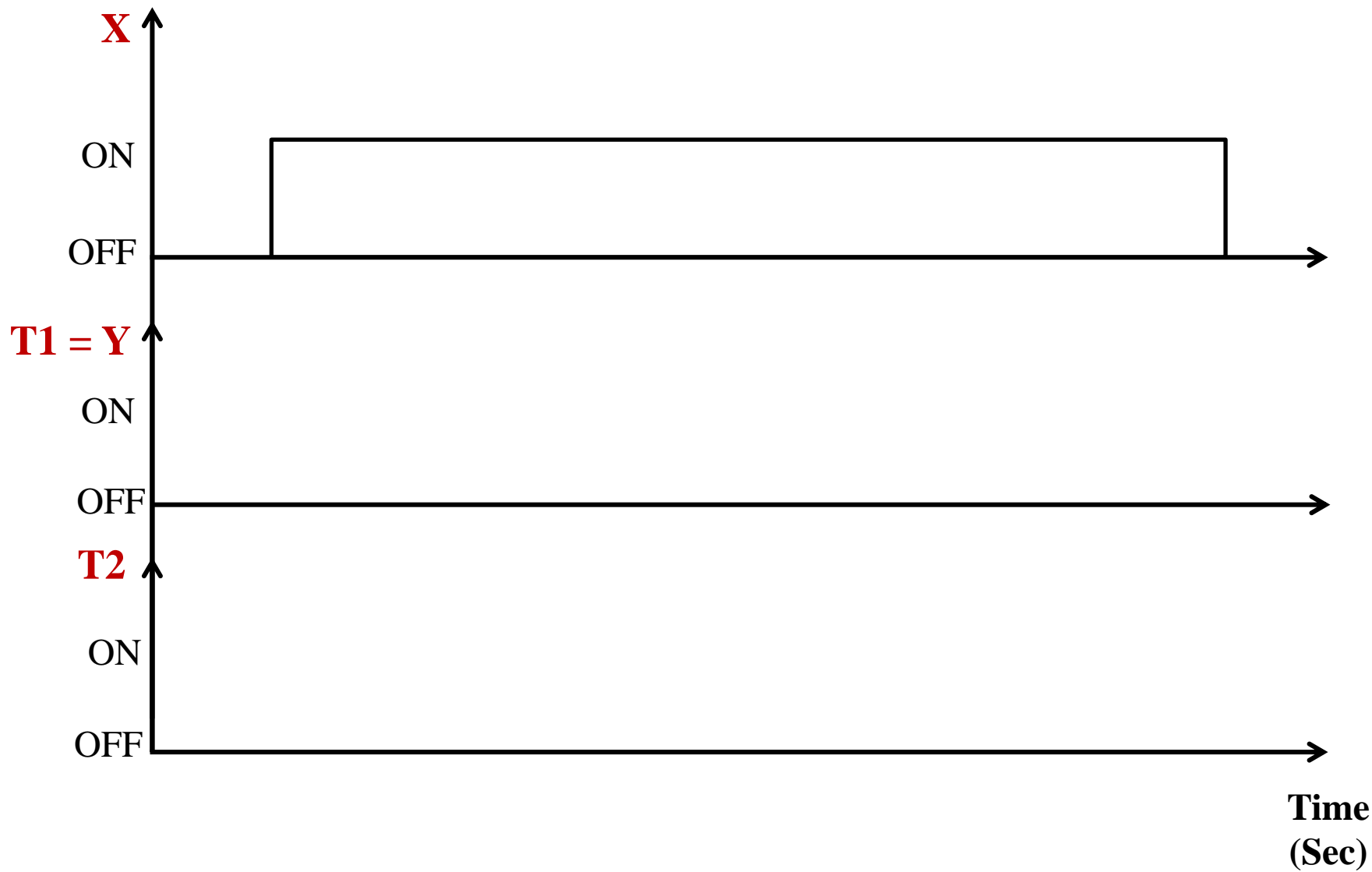

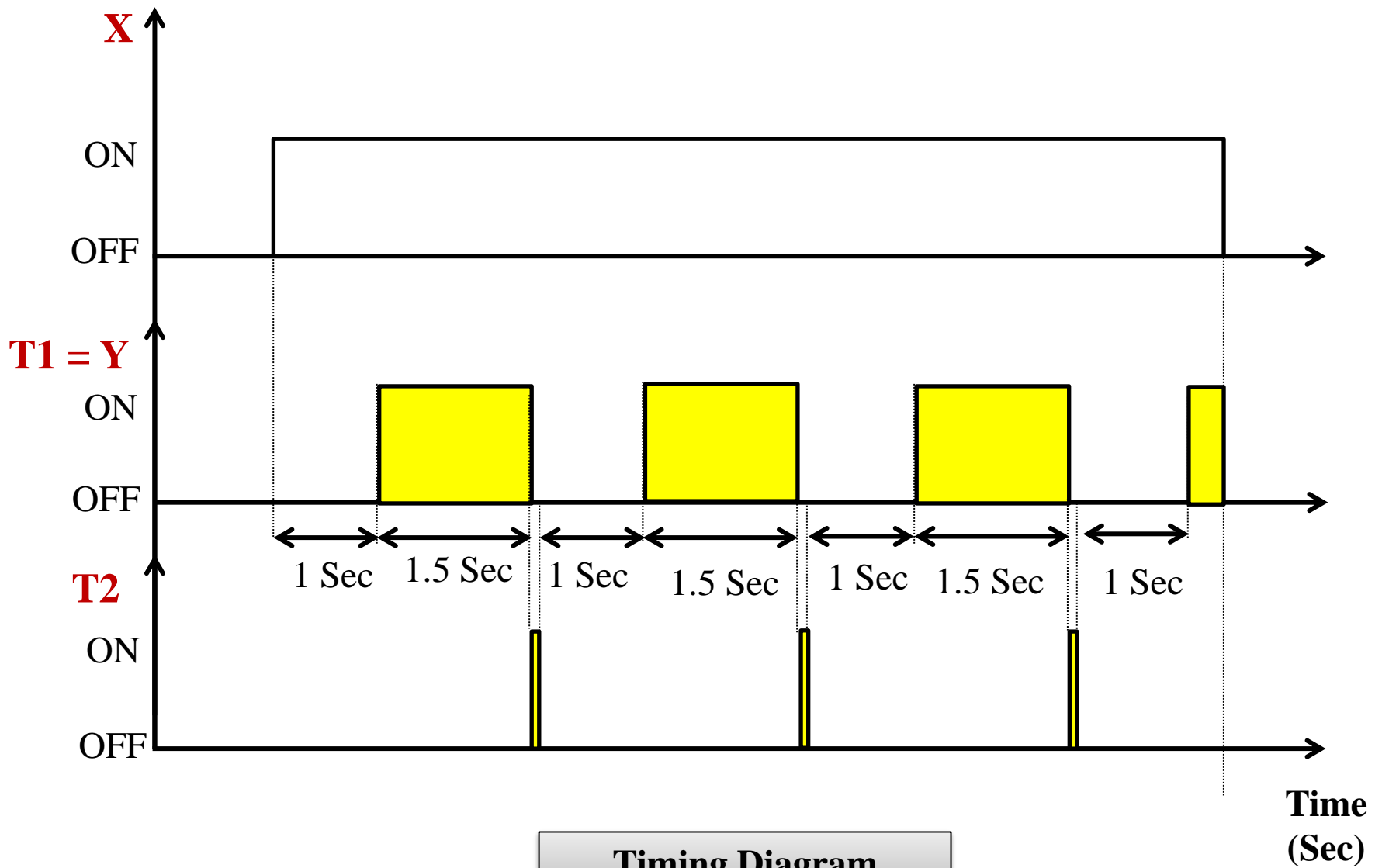


EX4: Level Control


- Write a ladder diagram program for the following system shown in the following figure. we want to fill tank1 and tank2 with water by the following sequence: When start switch is pressed, the valve (**V1**) opens to fill tank1 with water until it reaches to the desired level (via floating switch **LS1**).
- The valve (**V2**) waits 3 Sec, and then it opens to fill tank2 with water until it reaches to the desired level (via floating switch **LS2**).
- When tank2 is full, the system stops automatically, and an indicator lamp (**L**) is turned on to show that the process of filling the two tanks is ended.
- There exists a stop switch to end the process at any emergency time.

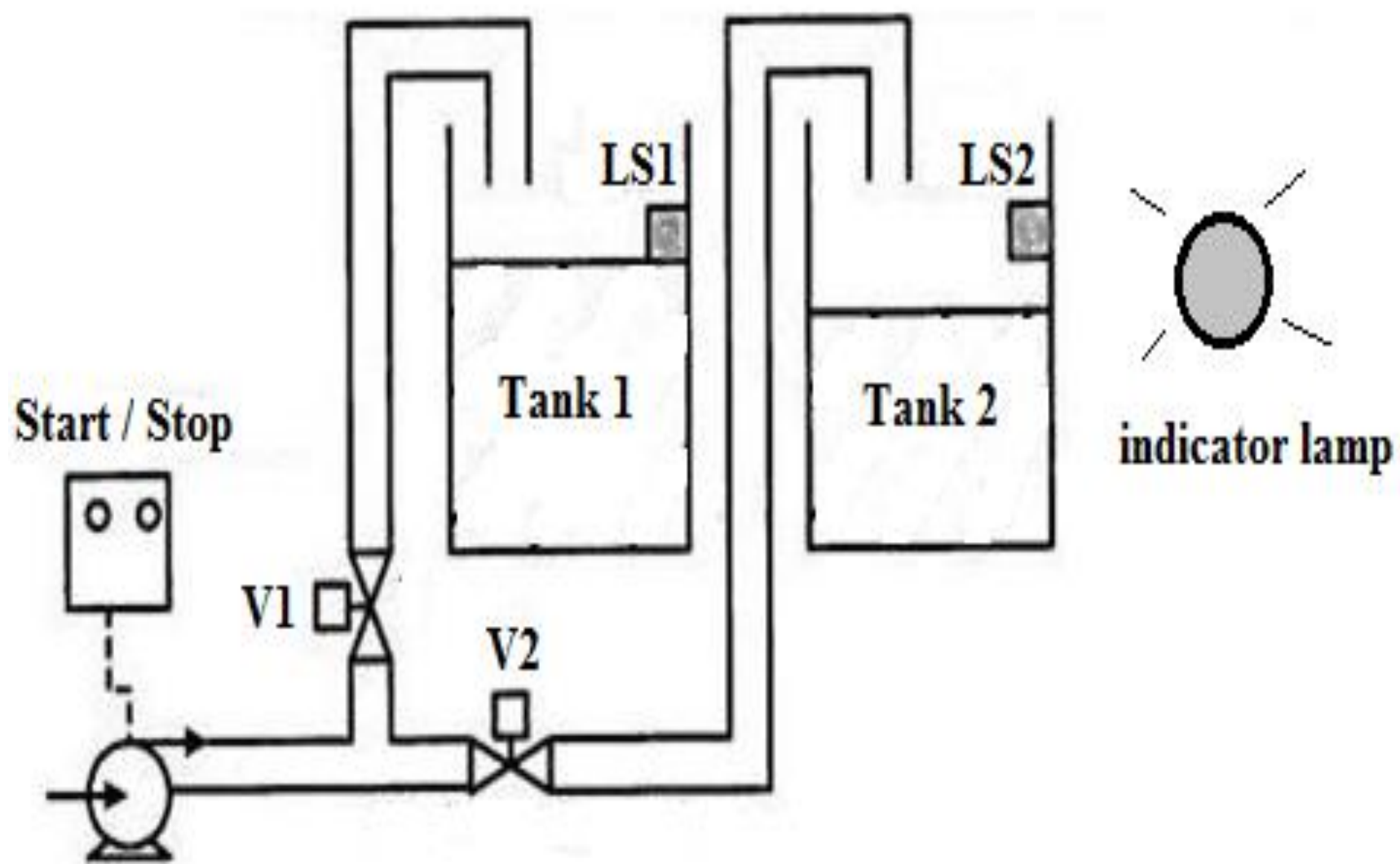

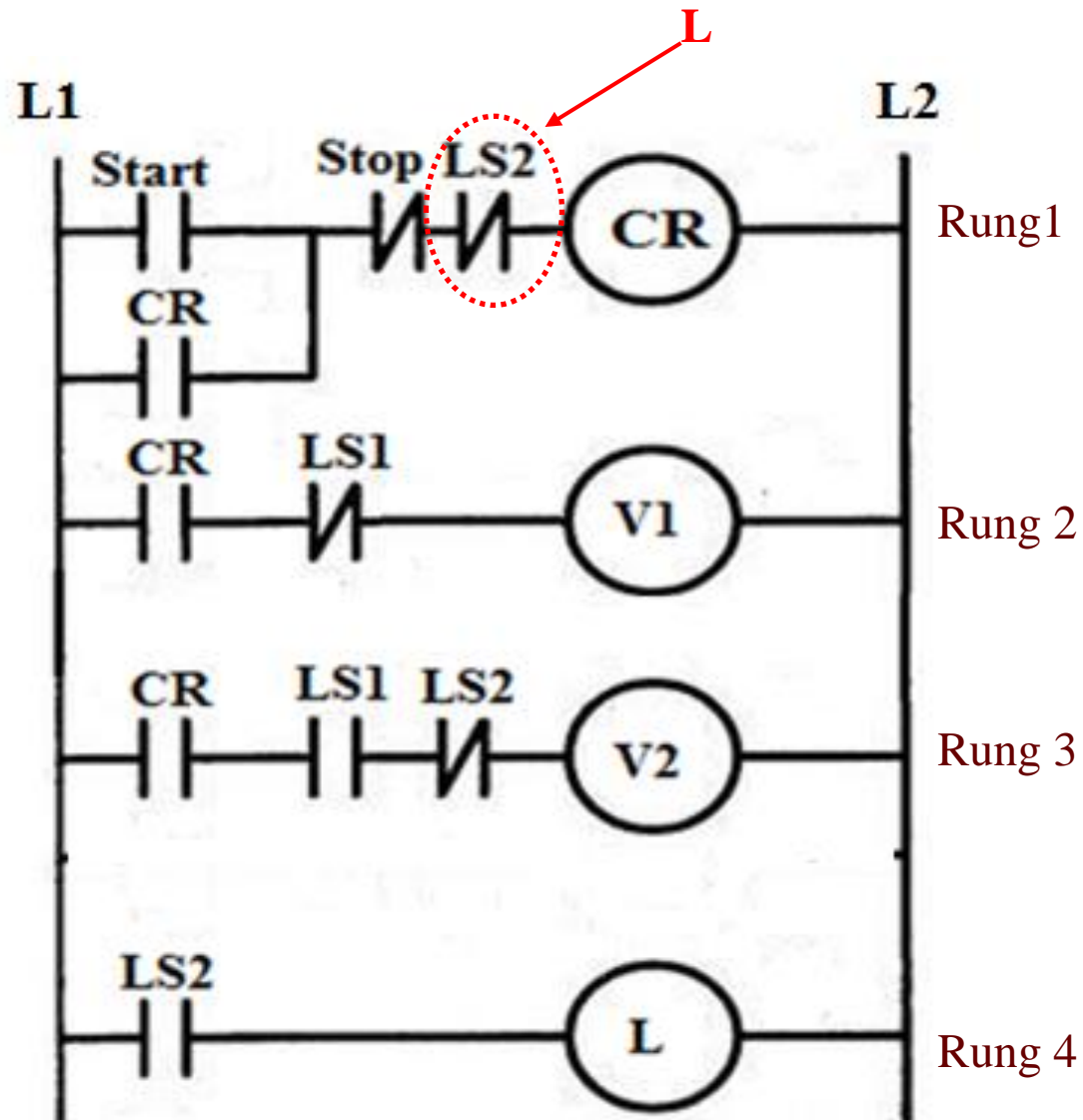- Remember, we have already solved this example before without using timer as:




**Solution
using timer**

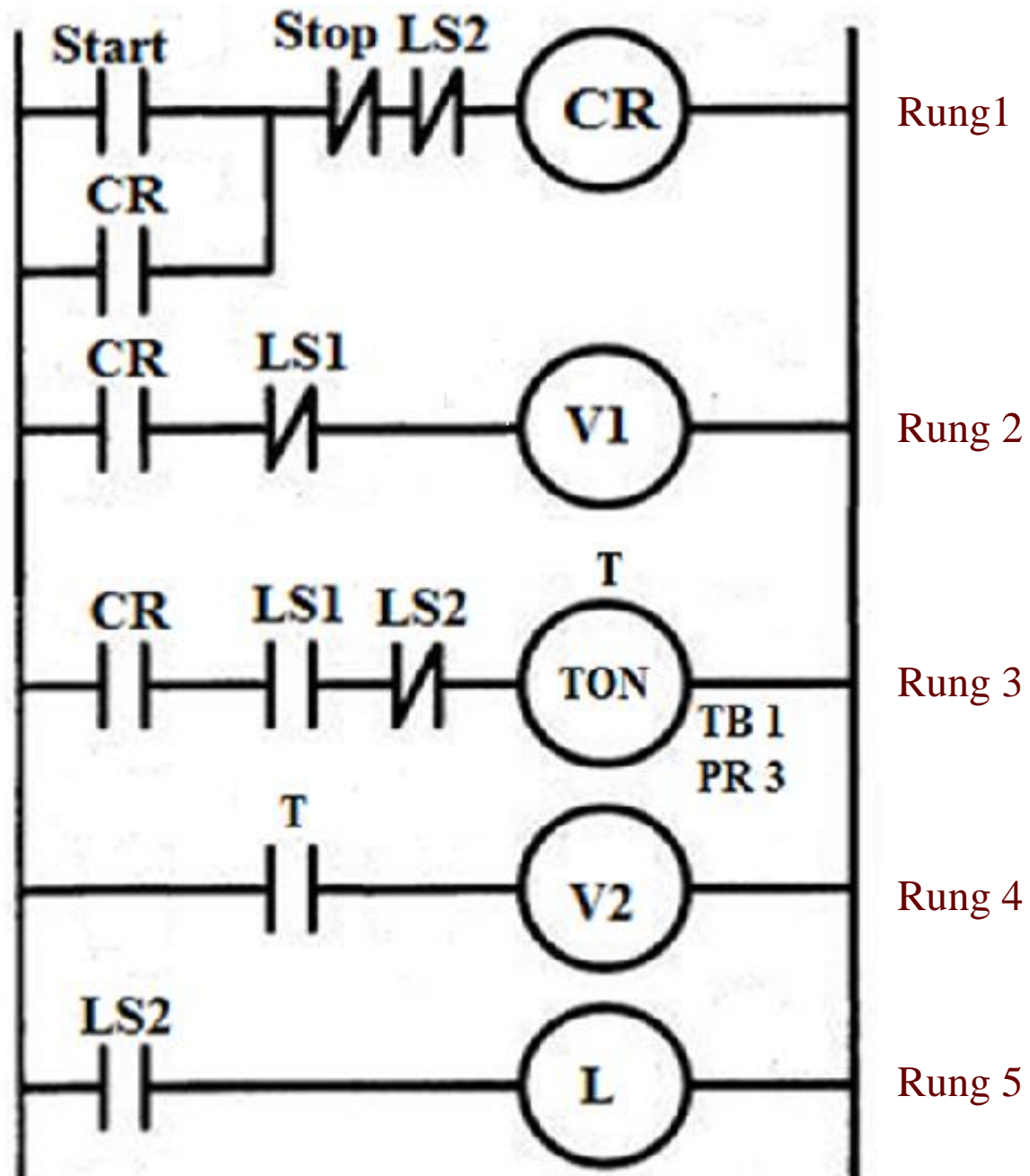

EX5: Level Control

In the following figure we want to fill tank1 and tank2 with water by the following sequence:


- When start switch is pressed, the valve (V1) opens to fill tank1 with water. The time required to fill tank1 is 6 Sec.
- After filling tank1, the valve (V2) waits 2 Sec and then it opens to fill tank2 with water. The time required to fill tank2 is 5 Sec.
- When tank2 is full, the system stops automatically, and an indicator lamp (L) is turned on to show that the process of filling the two tanks is ended.
- There exists a stop switch to end the process at any emergency time.

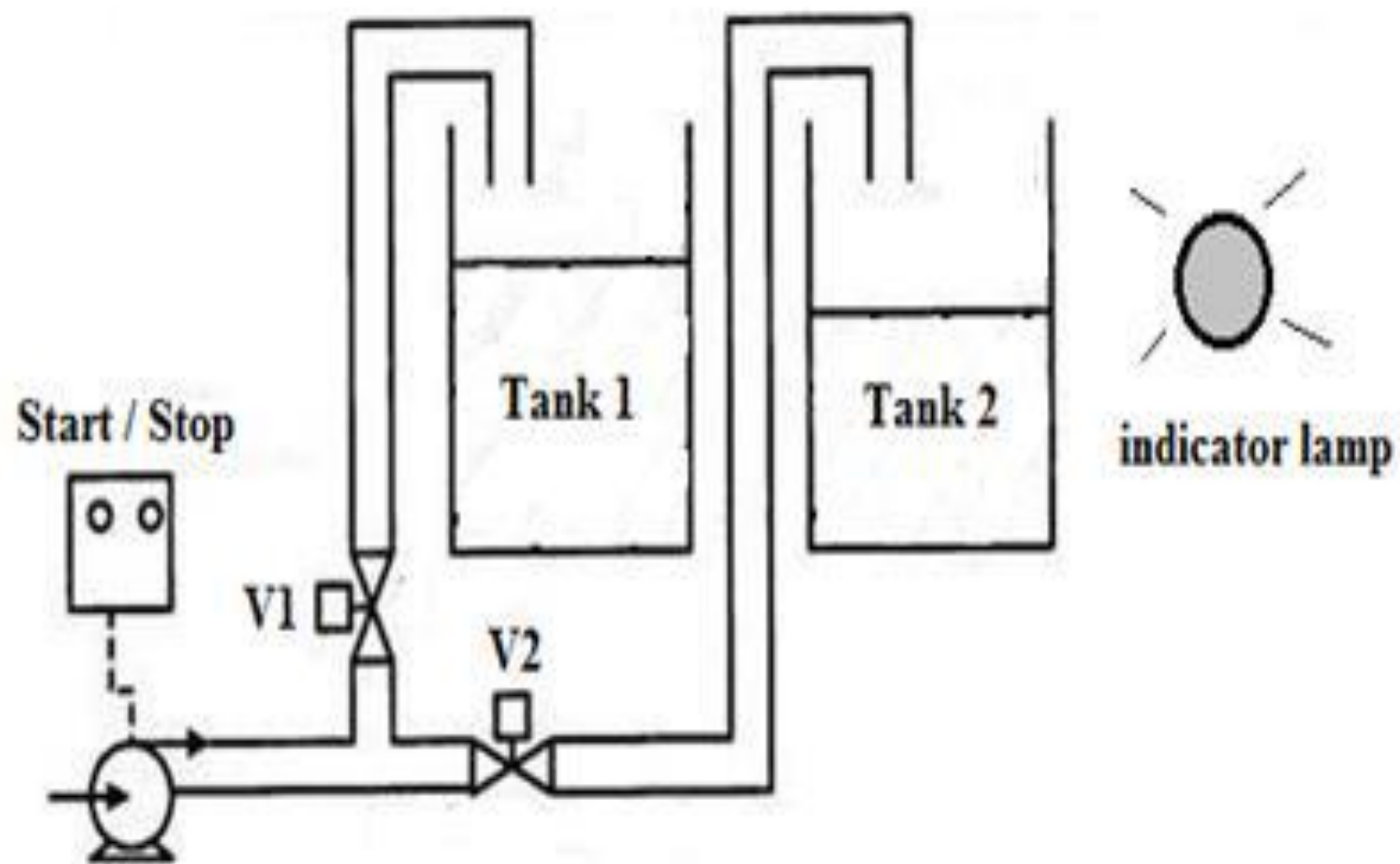

Solution

لضمان عدم
تشغيل V1 مرة
أخري بعد مرور
ال ٦ ثواني

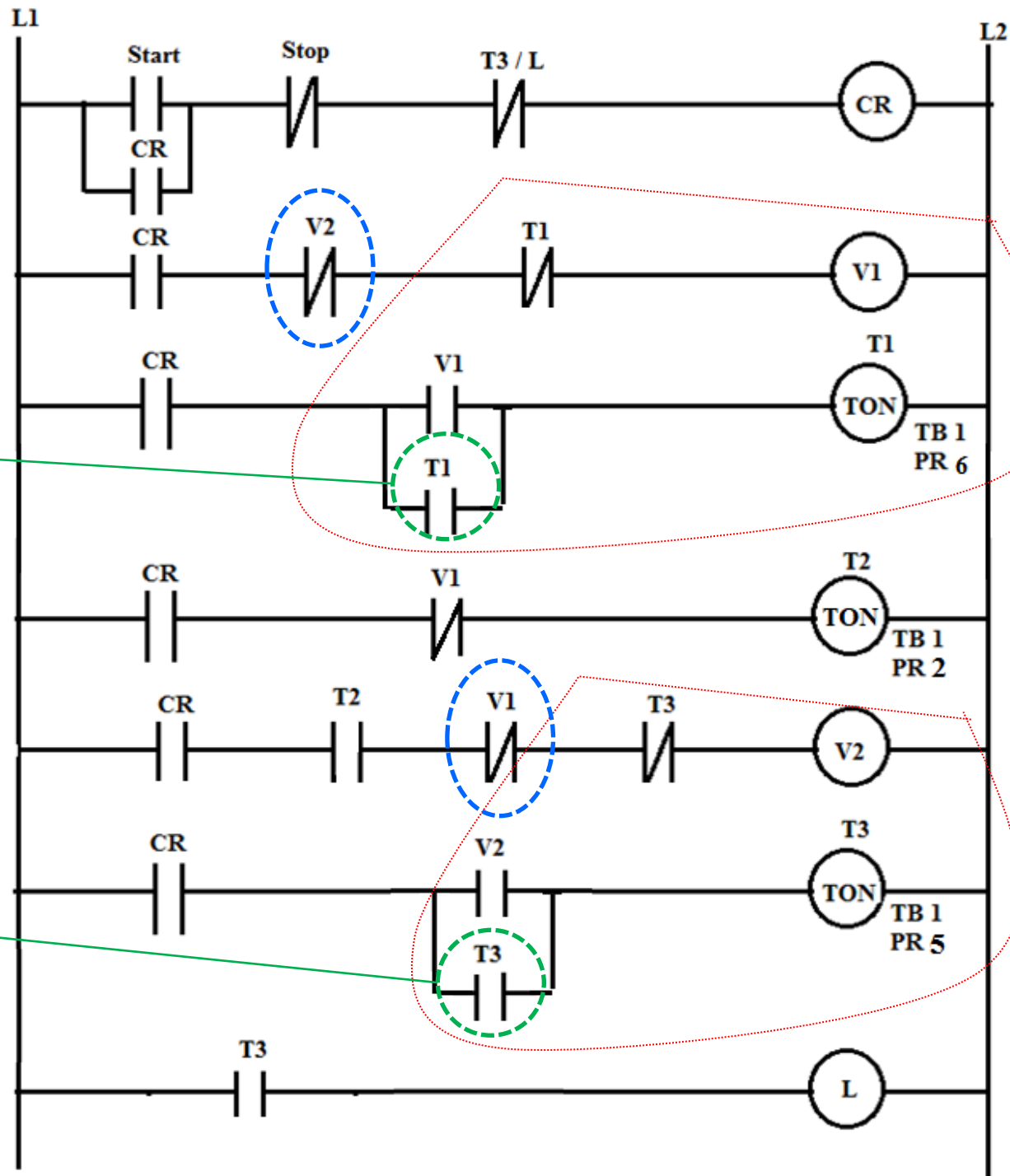
لضمان عدم
تشغيل V2 مرة
أخري بعد مرور
ال ٥ ثواني



يتحكم فى زمن
تشغيل V1

يتحكم فى زمن
تشغيل V2

Another solution

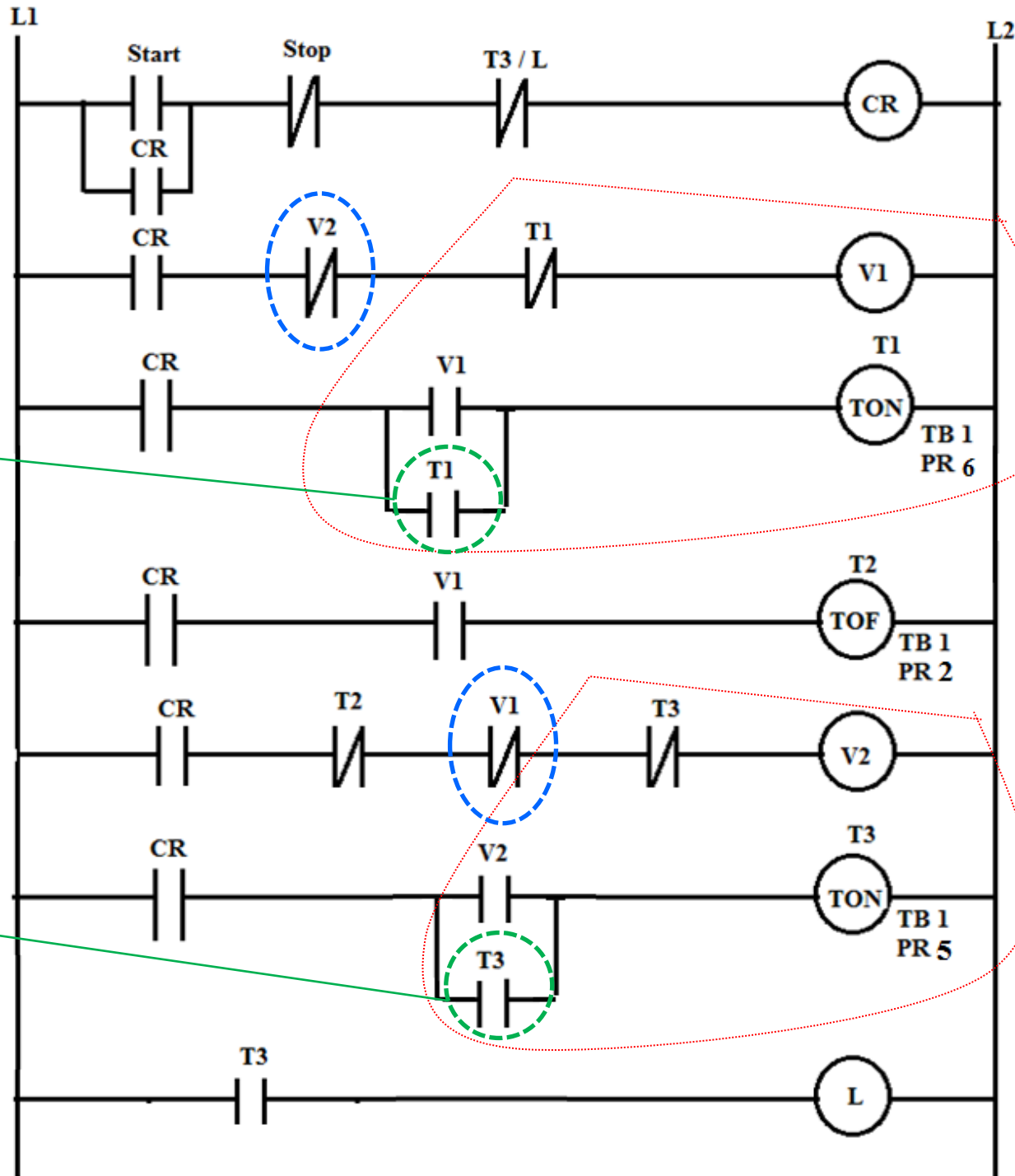

يتحكم في زمن
تشغيل V1


يتحكم في زمن
تشغيل V2

لضمان عدم
تشغيل V1 مرة
أخرى بعد مرور
ال ٦ ثواني

لضمان عدم
تشغيل V2 مرة
أخرى بعد مرور
ال ٥ ثواني

EX6: Production Line

- Draw a suitable ladder diagram program for a production line shown in the following figure. The sequences of its operation as follow:
 - 1) It detects the position of a bottle via a limit switch (**LS**), stops the motor (**M**) then, waits 4 sec and then opens the valve (**V**) to fill the bottle until a photo-sensor (**PS**) detects a filled condition.
 - 2) After the bottle is filled, waits 3 sec, then the motor (**M**) moves again to repeat these operations to the next bottle and so on.
- The production line should include start and stop push button switches to start and end these operations.

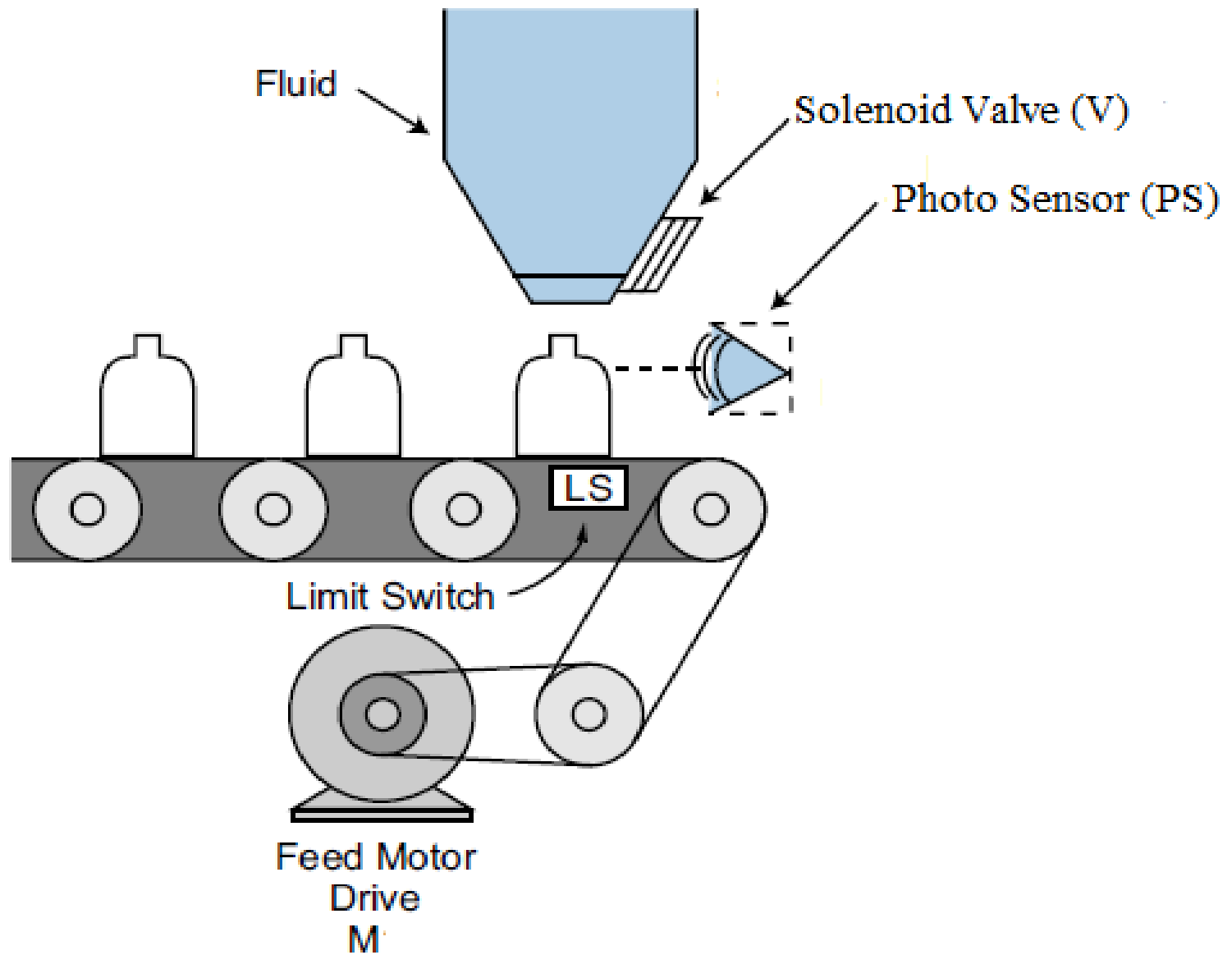

- We need the following inputs, outputs and internals:

Label	I/O
Start (NO Push button switch)	Inputs
Stop (NC Push button switch)	
LS	
PS	
M (Motor)	Outputs
V (Valve)	
CR	Internal relay / Internal output
T1 (4 sec TON)	Timers
T2 (3 sec TON)	

